

```
library ieee;
use ieee.std_logic_1164.all;

entity Q1 is
    port ( signal A, C, D, E, F : in std_logic;
          signal L : out std_logic);
end;

architecture df1 of Q1 is
    signal B, H, K, G, I, J : std_logic;
begin
    B <= not A;
    H <= B and C and D;
    G <= not F;
    I <= E or G;
    J <= not I;
    K <= H xor J;
    L <= not K;
end architecture df1;

architecture df2 of Q1 is
begin
    L <= ( ( (not A) and C and D) xor ( not (E or (not F)) ) );
end architecture df2;
```

DSDI HW10

